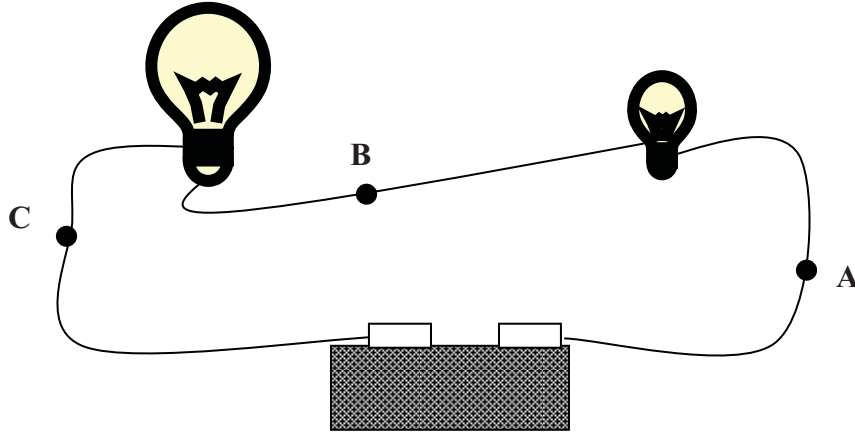


Pre-Lab 3

With a circuit similar to the one you had in the Final task of last week, but with two different light bulbs.



How do you expect the brightness of the light bulbs?

If you were to connect the ammeter into the circuit at points A, B and C, as shown below how would you expect the readings to compare and why?